

| made up of  |
|---|
| (a) (1) An LED TS , a N-type and p-type semiconductor   |
|   |
| fused together. The p-type 75 connected to the          |
| anode and the n-type connected to the cathode.          |
| a thin wire connects the p-type to the cathode.         |
| when a the semiconductor is fordwood brased,            |
| the electron flows and at the junction drops down       |
| from the conduction band to the valence band, releasing |
| its excess energy as light. a storice magnifying        |
| material covers the semiconductor to magnify the        |
| light emitted.  |
| <u> </u>  |
| ii) * An LED is much less likely to                     |
| break due to violent sharing,                           |
| a tost die 10 les solderig                              |
|   |
| components & wiving & prayile glass                     |
| composer to, so is used in aeroplanes                   |
| cre appropriace   |
|   |
| LED's draw unch los voltje                              |
| B Course to the second to the                           |



| appropriete as signal lights such      |
|--|
|  |
| as in a treffic light, which are       |
| constately require to be opporedj.     |
|  |
|  |
| * LED'S ARMBARA turning on \$          |
| Switching off times are much           |
| quicked thent that of light glab       |
| aver leght warras of eight globes, tus |
| water is the west was for they may     |
|  |
| ble useful as indication eights        |
| Such on in a hospital, madrag switchig |
| on when something is wary.             |
|  |
|  |
| It LED'S last for a meh longer         |
| period of time than ordinary light     |
| globes so in applications again        |
|  |
| Such as traffic lytte, where hegelonly |
| Menjing soms afficult, LED'S would     |
| be appropriate.                        |
| 77                                     |



| BOARD OF STUDIES                     |   |
|--------------------------------------|---|
| 1) As the illumination of light f    | falling upon the  |
|                                      |   |
|                                      |   |
|                                      | lux from the  |
| graph the resistance of the          | •   |
|                                      | . ,   |
| (i) V=IR                             | Data  |
| R-V                                  | TV= 12U   |
| - 12<br>- 48xw3                      | I= 4.8×w-3<br>R= 2500J2   |
| G=2500S                              | RIDR = 800R   |
| at Zlux RLDR = 800,2                 | RR= ? 17002   |
| PR = RT - RLOR                       | ·   |
| = 7500 - 800                         |   |
| RR = 1700SL                          |   |
| The resistance of the day is 1700sl. |   |
|                                      |   |
|                                      |   |
|                                      |   |
|                                      |   |
|                                      |   |
|                                      | (i) $V=IR$ $R=\frac{V}{I}$ $-\frac{12}{18xw^3}$ $R=2500\Omega$ $at Zlux R_{LDR}=800\Omega$ $\therefore R_R=R_I-R_{LDR}$ $=7500-800$ $R_R=1700\Omega$ $\therefore The veristance of the idea is 1700\Omega.$ |



| C(i) an    | ideal a | мp     | has     | infir | rite   | gain     |
|------------|---------|--------|---------|-------|--------|----------|
| an idea    | 1 amp   | a 150  | has     | infi  | nite   | input    |
| resistance | so that | the    | oculput | re51  | stance | (1)      |
| O. Input   | vollage | should | 4e      | 0 U   | for    | mertinan |
| gain.      |         | ·      |         |       |        |          |

| (1) | Vout | 2.0        |   |
|-----|------|------------|---|
|     | Vin  | = -50×1025 |   |
|     |      | -40 000    |   |
|     |      | 2 10,000   | • |

The output voltage is clipped secause the output voltage is clipped secause the input voltage has a greater range this is shown when imput voltage of 200 and 250 microvolt both produce output of -8 V. This would areate distortion from the output.



d) Thermionic devices were bulby, slow and complicated on large scales. Development and research led to the development of the tronsister which replaced the them thermionic devices. The transistor allowed adot more windows of oppurturity to be opened due to its small size and efficiency/reliability. It storted a rapid growth in electronics that relied on transistors as a building block. Computers benefited greatly as they could now be built smaller and quicker, resulting in a greater acceptance and wider use. With the development of integrated circuits which pack millions of transisturs into a small chip, Integrated

<sup>&</sup>gt; computers have become much faster and cheoper to produce.



circuits are now getting even smaller as new 0.13 micron processing plants are opening allowing transistors to be closer and smaller than over before. The IC has allowed computers to reach a cost accessible to the home user and has ment a great increase in computers and our reliance upon them. Unfortunatly thre are alimitations to the development of IC's. As they get smaller and smaller distances between the inhall components light common no longer be used to each Him. It's possible that in the feature x-rays will allow ICS to continue to shrink and contain more transistors. Due to our leavy relience on Ic's it is almost guaranteed that future research will allow their continued development or a solution to replace and improve upon them. But for the time being computers have readed speeds of 3GHZ thanks to the impact of IC's which is more speed then most computer softwere will need for a great fine to corne