

Question 17 (2 marks)


(a) Write an equation for Ohm's Law.

1

$$V = IR$$

(b) Calculate the current in the electrical circuit shown.

1

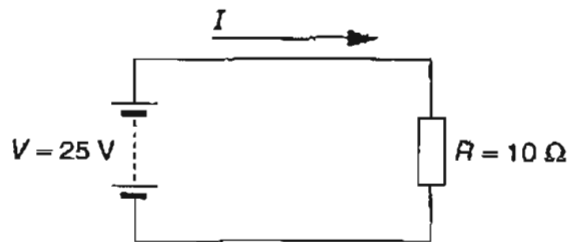

$$I = \frac{V}{R}$$

$$I = \frac{25}{10} \\ = 2.5$$