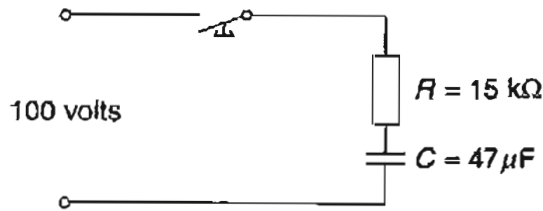


Question 20 (5 marks)

An electrical circuit is shown.



Calculate, showing all working:

- (a) the time constant for the circuit;

2

$$R = C t$$

$$\frac{15}{0.47} = \frac{0.47 \times t}{0.47} \quad \cancel{0.47} \quad t = 31.915$$

- (b) the maximum circuit current;

1

$$I = \frac{V}{R} \quad \frac{100}{15} = 6.6667$$

- (c) the value of resistance to be added to change the time constant to one second.

2

$$R = C t$$

$$R = 0.47 \times 1$$

$$R = 0.47 + 15$$

$$R = 15.47 \Omega$$