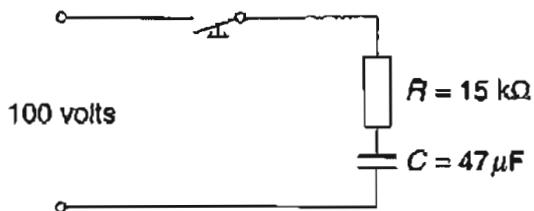


Question 20 (5 marks)

An electrical circuit is shown.



Calculate, showing all working:

- (a) the time constant for the circuit;

2

$$\tau = RC$$

$$= 15 \times 10^3 \times 47 \times 10^{-6}$$

$$= 15000 \times 0.705 \text{ seconds}$$

- (b) the maximum circuit current;

1

$$I = \frac{V}{IR} = \frac{100}{15000}$$

$$= 8.7 \times 10^{-3} \text{ (1.d.p.)}$$

- (c) the value of resistance to be added to change the time constant to one second.

2

$$22000 - 15000$$

$$= 7000 \Omega \text{ needs to be added}$$

to reach one second