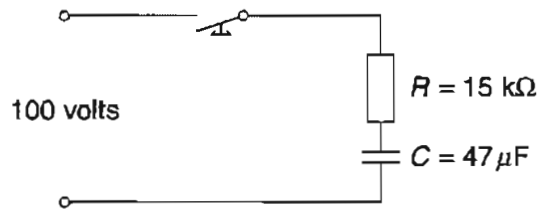


Question 20 (5 marks)

An electrical circuit is shown.



Calculate, showing all working:

- (a) the time constant for the circuit;

2

$$\begin{aligned} T &= RC \\ &= 15 \times 10^3 \times 47 \times 10^{-6} \\ &= 0.705 \text{ secs} \end{aligned}$$

- (b) the maximum circuit current;

1

$$\begin{aligned} I &= \frac{V}{R} = 6.6 \text{ mA} \\ &= \frac{100}{15 \times 10^3} \end{aligned}$$

- (c) the value of resistance to be added to change the time constant to one second.

2

$$\begin{aligned} 36.25 \times 10^3 \times 47 \times 10^{-6} \\ &= 1.705 \\ \therefore 20.25 \Omega \text{ needs to be added} \\ &\text{to increase time constant by one second.} \end{aligned}$$